


## Foreword

This application note is for MBI6001N1N, N1D, N2N and N2D. Based on the *MBI6001 Datasheet* and the attached *MBI6001 Iout Reference Table*, annexed to the product shipment, you may basically light on your LED loads. To further fine tune the operating current at various loads, please refer to this document.
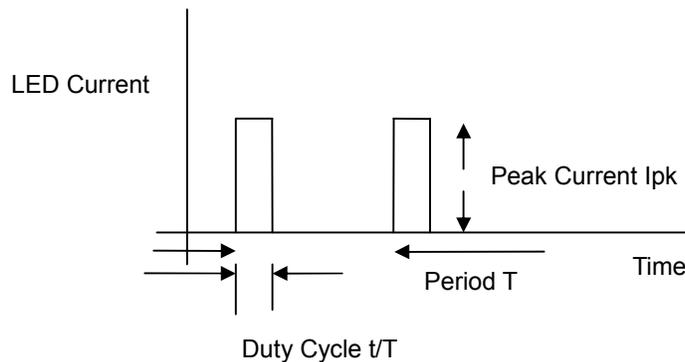
## Basics


MBI6001 series operate in a manner that they internally convert the incoming AC line power to a rectified and unregulated DC power and the internal circuitry further delivers the pulsed current to light on the LED load. N1x serves for 110 V AC and N2x for 220 V AC. The pulsed current with adequate pulse peak current and associated duty cycle gives a nominal Iout of average current that matches your LED load and light on your LEDs.

Refer to the *Typical Application Circuit*, the conceptual LED current could be depicted as:



Iout is defined as the average of LED Current, which is close to  $I_{pk} \times t/T$ .

### Typical Application Circuit

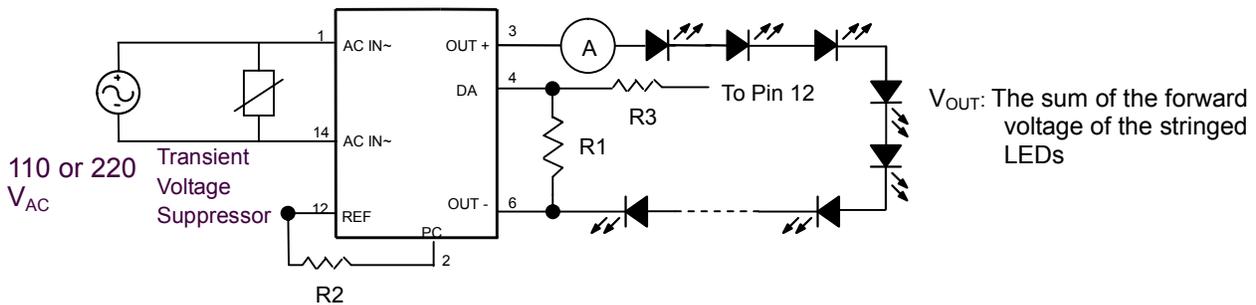

Note: There is no pin being connected to earth ground.

### Getting Started

To exploit MBI6001 with your LEDs, the vendor provides a default value of R1, R2, and R3 if any, to make LEDs lit. The following is to help you for fine adjustment by changing R1 and R2.

### The Numbers of LED Load

Before applying MBI6001, you need to know the characteristic of your LED load.

The LED load is suggested to be configured to a string of serial LED devices. When the LEDs are connected in series, the current flowing into the LEDs,  $I_F$ , must be equal to each other and equal brightness can be achieved. When LEDs are connected in series, the total forward voltage will be the sum of each  $V_F$ . When you apply N LEDs,  $N \times V_F$  will be the total forward voltage, where  $V_F$  is provided by LED vendors.

Now you can connect your LED load to MBI6001. Pin 3, OUT+, is connected to the anode of the string and Pin 6, OUT-, to the cathode. Since  $V_F$  is different for varieties of LEDs, MBI6001 characterizes the load by  $V_{OUT}$ , instead of  $V_F$ . For a specific LED, say, Green, White, etc., the  $V_F$  is determined. Then, applying N LEDs in series,  $N \times V_F$  will be perceived by MBI6001 as  $V_{OUT}$ .

To maintain the designated  $I_{OUT}$ , the voltage drop between Pin 3 and Pin 6,  $V_{OUT}$ , will automatically adopt the  $V_F$  change, where  $V_F$  is the Forward Voltage of LED devices which usually varies from lot to lot, even for a single type of LED..

However, due to the upper limit of input AC line power, such automatic adoption could only be guaranteed within a range. See Fig. 1-  $I_{OUT}$  vs.  $V_{OUT}$ , MBI6001 Datasheet. Within the range  $V_{OUT} = 10$  to 60 Volt, for MBI6001N1N,  $I_{OUT}$  will change less. It may thus be thought constant current.

For example, the  $V_F$  changes from 3.6 to 4.0 Volt for a single type of LED. When you connect 15 LEDs in series,  $V_{OUT}$  could range from  $15 \times 3.6$  to  $15 \times 4.0$  Volt, where the current is guaranteed invariant to  $V_F$  change.

Color	DC Forward Voltage $V_F$ [V]		Optical Power Output $P_O$ [mW]
	Typ.	Max.	Typ.
BLUE	3.6	4.0	6
GREEN	3.5	4.0	4
RED	1.9	2.4	2
WHITE	3.6	4.0	(4)**
Condition	$I_F=20mA$		$I_F=20mA$

### The Selection of LEDs

Usually, the commercial LEDs may work in two modes: DC current mode and pulsed current mode. In MBI6001 application, the LED should work in pulsed current mode. Hence, the maximum peak current should be taken into consideration. To achieve a typical  $I_{OUT}$  of 18 mA, a typical  $I_F(\text{peak})$  of 90 mA or larger is recommended. ( $I_F(\text{peak})$  is also denoted as Pulse Forward Current  $I_{FP}$ .) It implies the equivalent Duty Cycle  $t/T$  is around 20%. MBI6001 typically drives the LED at a pulse width of 1.66 ms, equivalently.

The reference LED maximum ratings are as below:

Color	DC Forward Current [mA]	Pulse Forward Current* <sup>n</sup> [mA]	DC Reverse Voltage [V]	Power Dissipation [mW]	Operating Temperature [°C]
BLUE	$I_F=30$	$I_{FP}=100$	$V_R=5$	$P_D=120$	Topr: -30 ~ +85
GREEN					
WHITE					
RED	$I_F=50$	$I_{FP}=200$	$V_R=5$	$P_D=120$	Topr: -30 ~ +85

\* Pulse width  $\leq 10ms$

### Setting the LED Currents by R1 and R2

When you have specified your LED, you may fine tune the operation current under MBI6001's limitations.

By adjusting R2, the I<sub>pk</sub> is defined. Please refer to the following tables:

**For MBI6001N1x:**

	Target I <sub>pk</sub>	Recommended R2
1.	40 mA	430 Ohm
2.	70 mA	100 Ohm
3.	90 mA	51 Ohm

**For MBI6001 N2x:**

	Target I <sub>pk</sub>	Recommended R2
1.	40 mA	Open
2.	70 mA	162 Ohm
3.	90 mA	91 Ohm

You may start the fine tuning with the recommended resistance of R1. See the I<sub>out</sub> Reference Table attached with shipment. Since I<sub>out</sub> is close to I<sub>pk</sub> x t / T, we may slightly adjust the Duty Cycle t/T to obtain various I<sub>out</sub>. To achieve a target I<sub>out</sub>, a measurement of I<sub>out</sub> is necessary. A simple hand-held multi-meter, which measures the pulsed LED current in a DC averaging manner, is connected in series with the LED string. The positive terminal is connected to Pin 3 OUT+ and the negative terminal to the anode of LED string. (See the Typical Application Circuit.) The reading on the multi-meter is what I<sub>out</sub> is defined in the datasheet. Since MBI6001 has a temperature correction in I<sub>out</sub>, the reading would only be significant 5 minutes after MBI6001 and LED load are powered.

You may now change slightly the resistance of R1 to adjust your I<sub>out</sub>. Usually, the smaller resistance of R1 you give, the smaller I<sub>out</sub> you obtain. The resistance range should not be large to adjust the I<sub>out</sub> exceeding 23 mA. The maximum load current I<sub>out</sub> is suggested to be 23 mA.

For example, MBI6001N1N with V<sub>OUT</sub>= 35 Volt, 110 Volt, under the condition R2 = 51 Ohm and I<sub>pk</sub> = 90 mA, you may result:

	R1	I <sub>out</sub>
1.	910K Ohm	19.18 mA
2.	953K Ohm	19.66 mA
3.	1000K Ohm	20.28 mA

The exact resistance of R1 (or R3) should be referred to the attached I<sub>out</sub> Reference Table, annexed to the product shipment

Please layout a vacancy for R3 on your PCB (printed circuit board), even you don't use R3 now. The R3 is reserved for extending the adjustment range of I<sub>out</sub>. For MBI6001N1N, it is open-circuit.

For another example, MBI6001N2N with V<sub>OUT</sub>= 70 Volt, 220 Volt, under the condition R2 = 91 Ohm and I<sub>pk</sub> = 90 mA, you may result:

	R3	I <sub>out</sub>
1.	100K Ohm	15.5 mA
2.	51K Ohm	16.5 mA
3.	43K Ohm	17.1 mA

In this case, you use R3 instead of R1. R1 is left open-circuit.

### **The Limitation of MBI6001**

Although you may adjust the resistance of R2, the maximum load current I<sub>out</sub> is suggested to be 23 mA. Beyond 23 mA, additional heat is a concern.

Theoretically, MBI6001 may serve with wide ranges of Peak Current I<sub>pk</sub> and Duty Cycle t/T. However, a physical limit gives a constraint, the heat dissipation. MBI6001 endures a large voltage drop across the AC line power and the LED loads. The voltage drop and the current passed through cause a power dissipation which releases in a form of heat. Larger the current is delivered, hotter MBI6001 will be. Typically, MBI6001 dissipates 0.6 Watt to 1 Watt. You have to estimate the application environment that can dissipate the same heat to maintain an adequate temperature around the surface of MBI6001. In our typical application, the temperature at the surface of package under the free air, T<sub>a</sub> = 25°C, is measured as below 55°C, for MBI6001N1N, where a thermal couple with a multi-meter is applied. Please refer to Fig. 2- Temp. vs. V<sub>OUT</sub> in MBI6001 Datasheet. Likewise, 70°C is for MBI6001N2N.

Sometimes, T<sub>a</sub> = 25°C cannot be provided in your application. Then you will need to condition the heat dissipation.

To achieve conditioned heat dissipation, thermally conductive adhesives or silicone are recommended to fill the clearance between the MBI6001 package and the outer thermal conducting surface. The clearance is usually a poor thermal conductor. When the clearance is filled with the thermally conductive adhesive, the thermal conductivity is thus enhanced and suppresses the temperature increase on the MBI6001.

For example, <http://www.loctite.com/>, thermally conductive adhesive vendor is referenced. See also KE4560G and BB-1000 from [http://www.sunnico.com.tw/index\\_a.htm](http://www.sunnico.com.tw/index_a.htm).

When the thermally conductive adhesive is applied and your product is sealed, it will be hard to rework your product. You should carefully test the reliability before mass production.

## The safety

MBI6001 series are certified by UL and CE.

To prevent from electrical shock from the outdoor AC line power, a surge absorber or transient voltage suppressor is necessary to be connected in parallel to the Pin 1 and Pin 14. The maximum rating for AC line input is 400V, transient. The referenced surge absorbers or transient voltage suppressors (TVS) are:

P4KE Series from <http://www.panjit.com.tw/products.html>, or, from <http://www.ts.com.tw/semi/index.html>.


The Maximum Clamping Voltage,  $V_c$ , or Maximum Breakdown Voltage,  $V_{br}$ , is chosen as less than 400V (Transient). The Stand-off Voltage is chosen as larger than 170V ( $120V \times 1.414$ ) for 110V line power and 340 ( $240V \times 1.414$ ) for 220V line power.

You may use PK4E200A for nominal 110VAC and PK4E400A for nominal 220VAC.

Since MBI6001 is not isolated from the AC line power, it is strictly forbidden for connecting any portion of the application circuit to the global earth ground. This is especially critical for any measurement instruments which are powered by AC line. Hand-held or portable multi-meters are recommended.

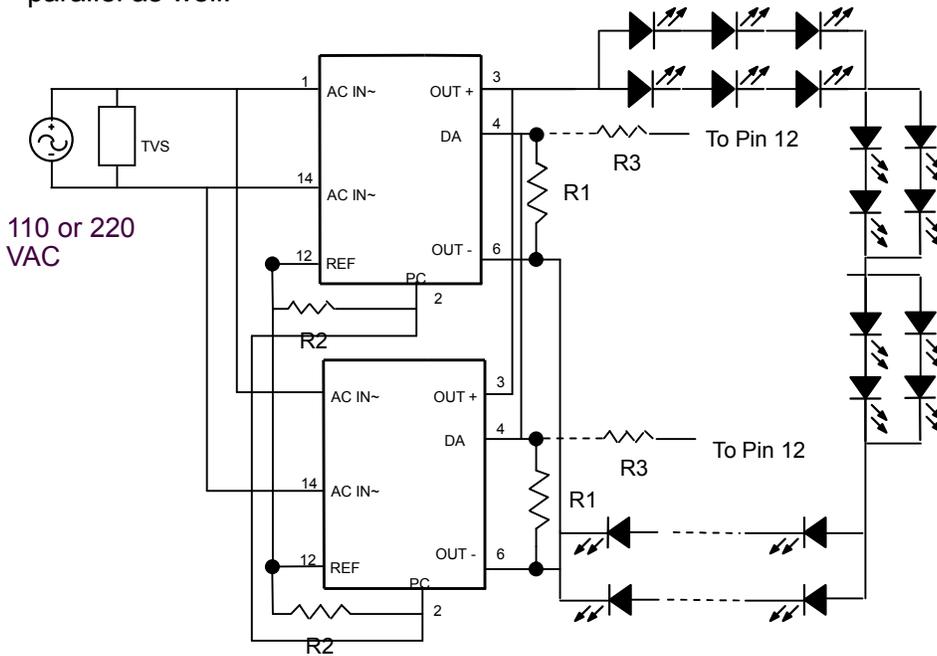**Extended Application**

In some cases, the configuration of LED load will not be a simple string. To extend for larger lout or to avoid the accidental LED failure, usually open-circuit, that disables the current path for whole LED string, you could purposely select a sort of LED of higher  $I_F$  (peak) which endures larger  $I_{pk}$ , or you may connect your LED string in parallel and connect MBI6001 in parallel as well.



The selection of R1, and R2 is as defined as in the case of single string. Equivalently, the two MBI6001s are connected like piggy-back.

For example, when your target lout is 54 mA, three times of recommended 18mA, you may connect 3 MBI6001 ICs in parallel. The selection of R1 and R2, is just the same as you select for 18 mA for each MBI6001. When total lout is 54 mA, the total Peak Current  $I_{pk}$  will usually be  $90 \text{ mA} \times 3 = 270 \text{ mA}$ . Accordingly, you shall select adequate  $I_F(\text{peak})$  of LEDs, which is larger than 270 mA.

In the case of using single LED string of  $I_F(\text{peak}) = 80 \text{ mA}$  while expecting  $I_{out} = 28 \text{ mA}$ , the target lout exceeds the upper limit, 23 mA. You may use two MBI6001 ICs in parallel and make each MBI6001 deliver  $I_{out} = 14 \text{ mA}$  by setting R1 or R3.  $I_{out} = 14 \text{ mA}$  is beneath MBI6001 limit. The  $I_{pk}$  for each would be set to 40 mA not 80 mA. (Concerning the LEDs, the equivalent duty cycle would be  $28 / 80 = 35\%$  which is usually not guaranteed by LED vendors and is larger than our suggestion, 20%.)

**Measuring the load current by using Oscilloscopes**

It is not suggested to measure the I<sub>out</sub> by using oscilloscopes. It is always a hazard if you erroneously connect the reference claps to the application circuit.

If you have to know the current flowing through the LED load, a current probe is the most common means.

If you have to know the current flowing through the LED load and you don't have a current probe, you may insert a 1-Ohm resistor in series with LED string and measure the voltage across the 1-Ohm resistor. When measuring the voltage with a regular voltage probe, you put the probe tip on one end of the resistor and put the reference clap on the other. You may obtain the voltage waveform and thus the current waveform.

Caution: Never measure your application circuit by using more than two channels from your oscilloscope simultaneously. It will be a risk to falsely connect your two reference claps to two nodes with very high voltage drop. The false connection will cause either the damage of your scope or your application circuit.